

Home Assignment 4, IE1206 & IF1330, VT2020

Problem 1


Per-Erik connected a load resistor R_L to a battery rated to be 9V. He measured the voltage (V_L) over the load resistor for different values of R_L . The measured data is shown in the table below.



R_L	100 k Ω	10 k Ω	1 k Ω	177 Ω	38 Ω
V_L	9.16	9.15	9.01	8.58	7.28

Determine the Thevenin equivalent of the 9V battery.


Problem 2

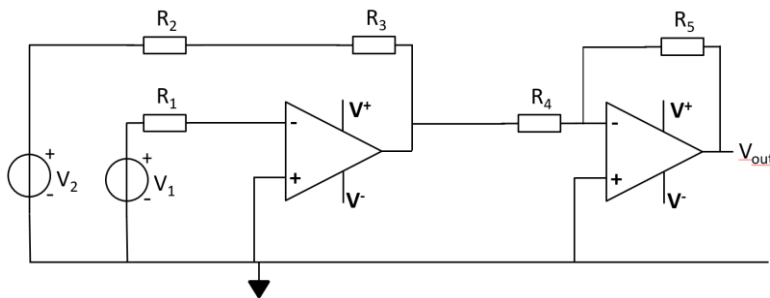

A) Determine the output voltage V_{out} as a function of $V_1, V_2, R_1, R_2, R_3, R_4$ and R_5 . Assume the operational amplifiers are ideal and operates in the linear region.


B) Determine V_{out} if $V_1=2$ V, $V_2=3$ V and $R_1=R_2=R_3=R_4=R_5=2$ k Ω .

Problem 3

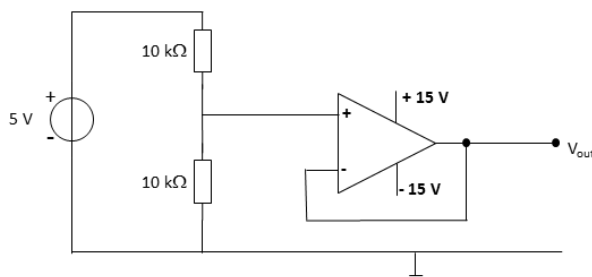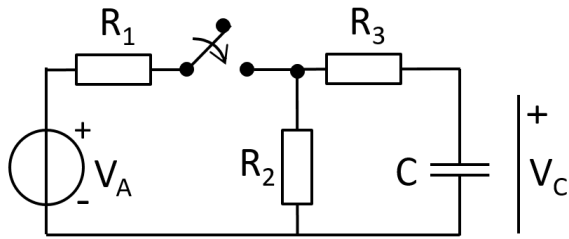


(A) Determine the output voltage V_{out} assuming that the op-amp operates in the linear region and is ideal.

(B) What is the function of the op-amp (think about the op-amp input resistance)? What function does the circuit perform?


Problem 4

The switch has been open for a long time. At time $t=0$ s the switch closes. Determine the voltage over the capacitor V_C at time $t=2$ ms. $V_A=6$ V, $R_1=R_2=10$ k Ω , $R_3=5$ k Ω and $C=100$ nF.

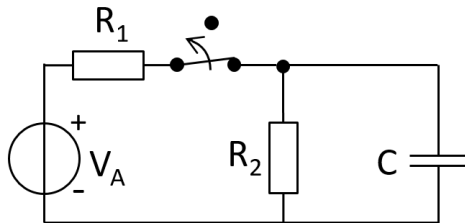Problem 5

The switch has been closed for a long time. At $t=0$ s the switch opens. $V_A=5$ V, $R_1=1$ k Ω , $R_2=4$ k Ω and $C=2.5$ nF.

- A) What is the energy stored in the capacitor at $t=0$ s?
- B) What is the energy stored in the capacitor at $t=10$ μ s?

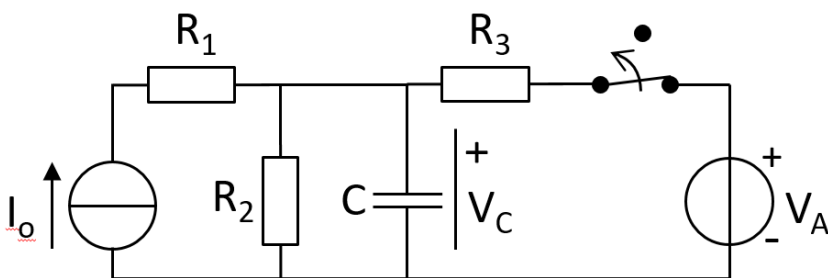Problem 6

The switch has been closed for a long time. At time $t=1$ μ s the switch opens. $R_1=10$ k Ω , $R_2=R_3=1$ k Ω , $C=2$ nF, $I_0=2$ mA and $V_A=6$ V. Plot $V_C(t)$ in the interval $0 < t < 7$ μ s.