Inbyggd elektronik 2018-04-17 #8

Up to now, everything has been static (DC) No time dependence.

Module 3: C, L, V(b), i(t)

- · Capacitance and inductance are geometrical effects
- · They introduce/cause time delays in circuits.

Capacitance $Q = C \cdot V$ [F] Farad

Any separation of charge will generate an electric field between the charges. >> The charges are at different electrical potential.

Inductance Pr=L·I

PB is the magnetic flux. Any moving charges (i.e current) will set up a magnetic field.

[H] Henry

· Faradays induction law states that a time varying magnetic field induces a voltage, (and thus a current), in a conductor.

Capacitance and inductance effects are "everywhere" but can often be negliable. For example two wires

can be

modeled as

A Capaticor is a device designed to have a large capacitance - Two parallell plates seperated by a thin insulator has a high capacitance (= EA E[FM]

An Inductor is a device designed to have a large inductance - A conducting wire formed like a coil 1 has a high inductance L= po nºAL

Two new linear circuit elements Capacitor and Inductor

Resistor

Capacitor C 类")"Ve

Inductor

ic=CdVe

IL is continous

since VL +00

Vp=RIp

Store/release electrical energy (from/to circuit) in/from a magnetic field in the coil.

energy to

heat/light

Vc is continous since ic = 00 Converts electrical Store/release electrical energy (from/to circuit) in/from an electric field between the two metal plates.

NOTE f(x+y)=f(x)+f(y) additivity f(ax) = af(x) homogenity This is called a linear map or that the function is linear.

n=turns/unit length

Resistor

Inductor

No energy is stored

Capacitor $E = C \frac{V_c^2}{2}$

E= L 10

 $P = \frac{dE}{dt} = CV_c \frac{dV_c}{dt} = i_cV_c$ $P = \frac{dE}{dt} = Li_c \cdot \frac{dic}{dt} = i_cV_c$