



KTH Informations- och  
kommunikationsteknik

# Written exam

## IE1206 Embedded Electronics

## IF1330 Electrical principles

### Friday 17/8 2018 08.00-12.00

---

### General Information

Examiner: Carl-Mikael Zetterling

Responsible teacher at exam: Per-Erik Hellström 08-790 43 25

**All sheets** that are handed in need **your name and personal number** written on them.

**Mark every sheet** with the **problem it deals** with.

**You cannot have more than one problem per sheet.**

### Aids: Calculator

The exam consists of 8 problems (5 points each) distributed over the 4 modules in the course:

Module 1: problem 1 and 2

Module 2: problem 3 and 4

Module 3: problem 5 and 6


Module 4: problem 7 and 8

To **pass the exam** requires at least **2 points** from each module and preliminary **20 points** in total.


**Grades** are given as follows:

Points	<20	20-23	24-27	28-31	32-35	36-40
Grades	F	E	D	C	B	A

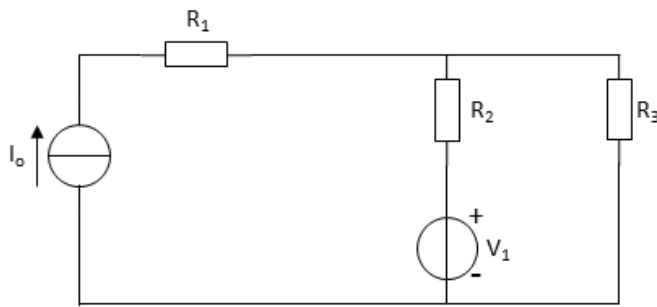
1. Determine the electrical power consumed in  $R_3$ .  
 $R_1=10\text{ k}\Omega$ ,  $R_2=0.4\text{ k}\Omega$ ,  $R_3=2\text{ k}\Omega$ ,  $V_1=3.2\text{ V}$ ,  $I_o=7\text{ mA}$ .



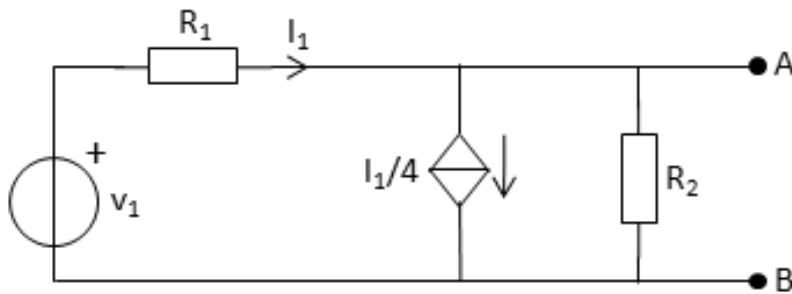2. Determine the Thevenin equivalent circuit seen at A-B.  
 $V_1=6\text{ V}$ ,  $R_1=1.5\text{ k}\Omega$ ,  $R_2=4\text{ k}\Omega$ .



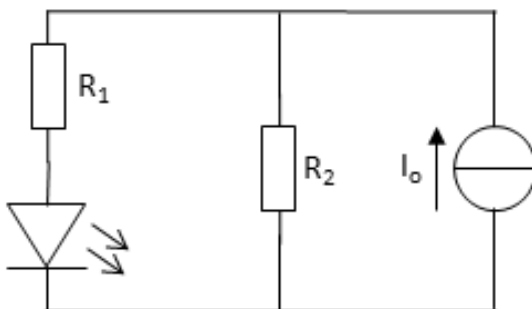
3. The light emitting diode (LED) has a threshold voltage  $V_T=2.0\text{ V}$ .  $R_1=1\text{ k}\Omega$  and  $R_2=2\text{ k}\Omega$ . Determine the current  $I_o$  needed to have a current of  $1\text{ mA}$  flowing through the LED so that it emits light brightly.



4. Assume the operational amplifier is ideal.

(A) Assuming operation in the linear region, derive an expression for  $V_{out}$  as a function of  $V_{in}$ ,  $R_1$  and  $R_2$ .

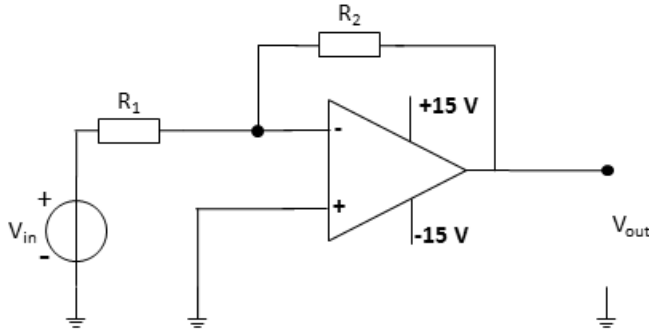
(B) Within what voltage range must  $V_{in}$  be to assure that the operational amplifier operates in the linear region?  $R_1=1\text{ k}\Omega$  and  $R_2=4\text{ k}\Omega$



5. In the circuit below  $V_o=3\text{ V}$ ,  $R_1=1\text{ k}\Omega$ ,  $R_2=2\text{ k}\Omega$ ,  $R_3=3\text{ k}\Omega$  and  $C=10\text{ nF}$ .

(A) The switch has been open for a long time. Calculate the RC time constant for charging up ( $\tau_{up}$ ) the capacitor when the switch closes.


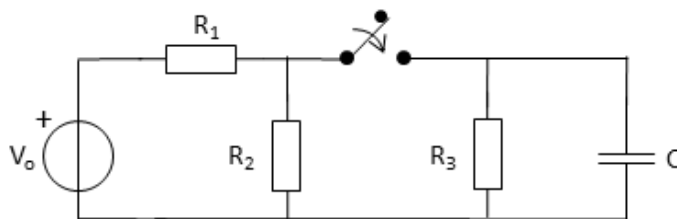
(B) The switch has been closed for a long time. Calculate the RC time constant for discharging ( $\tau_{down}$ ) the capacitor when the switch opens.




6. The current source in the circuit generates the current pulse shown in the figure below.

(A) Derive a numerical expression for the voltage over the inductor,  $V_L(t)$ , in the interval  $0 < t < 25\text{ }\mu\text{s}$ .

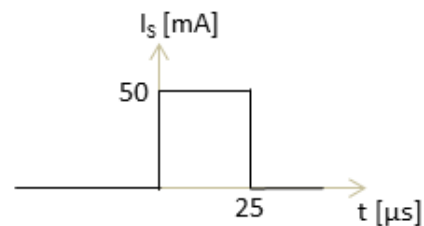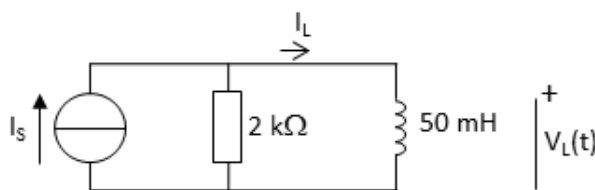(B) What is the energy stored in the inductor at  $t=25\text{ }\mu\text{s}$ ?



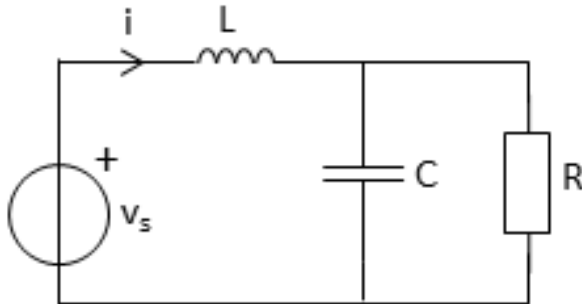7. (A) Derive an expression for the impedance ( $Z$ ) as a function of the angular frequency ( $\omega$ ) seen by the voltage source  $v_s$ .
- (B) Determine  $i(t)$  when the steady-state voltage source  $v_s = \sqrt{2}\cos(\omega t)$ ,  $L = 1$  H,  $\omega = 1000$  rad/s,  $R = 1$  k $\Omega$  and  $C = 1$   $\mu$ F.



8.  $v_{in}(t)$  is a steady-state cosine voltage source with amplitude  $A$  and frequency  $\omega$ .
- (A) Derive a complex expression for  $\frac{\hat{v}_{out}}{\hat{v}_{in}}$  that include  $\omega$ ,  $R$  and  $L$ .
- (B) What type of filter function does the circuit perform? Motivate your answer.

