



Written exam

IE1206 Embedded Electronics

IF1330 Electrical principles

Monday 3/6 2019 14.00-18.00

General Information

Examiner: Carl-Mikael Zetterling

Responsible teacher at exam: Per-Erik Hellström 08-790 43 25

All sheets that are handed in need **your name and personal number** written on them.

Mark every sheet with the **problem it deals with**.

You cannot have more than one problem per sheet.

Aids: Calculator

The exam consists of 8 problems (5 points each) distributed over the 4 modules in the course:

Module 1: problem 1 and 2

Module 2: problem 3 and 4

Module 3: problem 5 and 6


Module 4: problem 7 and 8

To **pass the exam** requires at least **2 points** from each module and preliminary **20 points** in total.


Grades are given as follows:

Points	<20	20-23	24-27	28-31	32-35	36-40
Grades	F	E	D	C	B	A

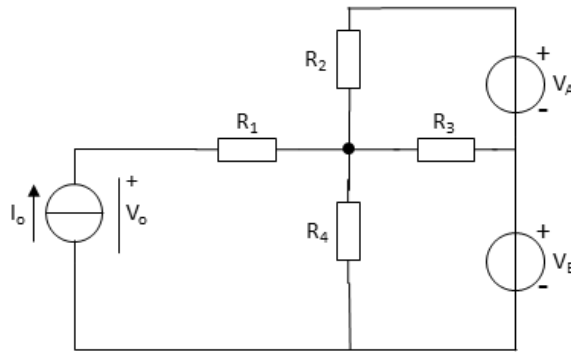
1. Determine the voltage V_o over the current source.
 $R_1=1\text{ k}\Omega$, $R_2=3\text{ k}\Omega$, $R_3=2\text{ k}\Omega$, $R_4=6\text{ k}\Omega$, $I_o=1\text{ mA}$, $V_A=1\text{ V}$, $V_B=5\text{ V}$.



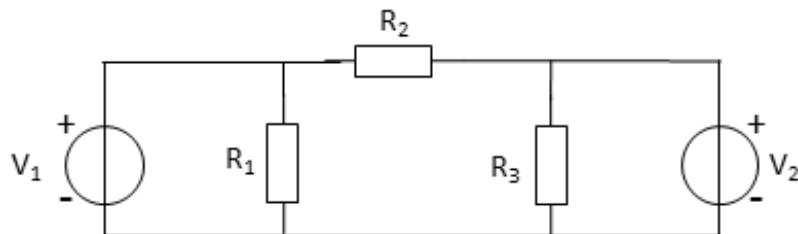2. $V_1=2\text{ V}$, $V_2=4\text{ V}$, $R_1=2\text{ k}\Omega$, $R_2=8\text{ k}\Omega$, $R_3=4\text{ k}\Omega$.
 (A) Determine the power consumed in R_2 .
 (B) What is the total power delivered by the voltage sources to the resistors?



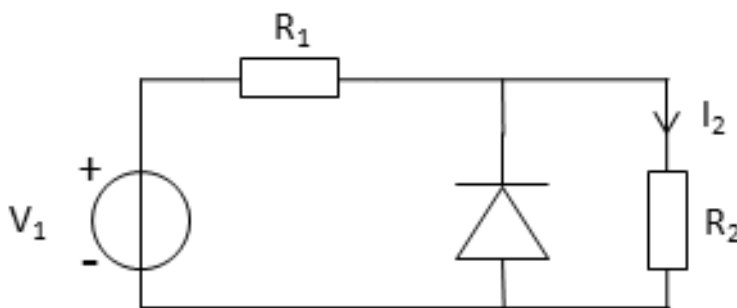
3. Determine the current I_2 . $V_1=4\text{ V}$, $R_1=10\text{ k}\Omega$ and $R_2=30\text{ k}\Omega$.




4. Assume that the operational amplifier is ideal.

(A) Express V_{out} as function of V_{in} , R_1 and R_2 when the operational amplifier works in the linear region.

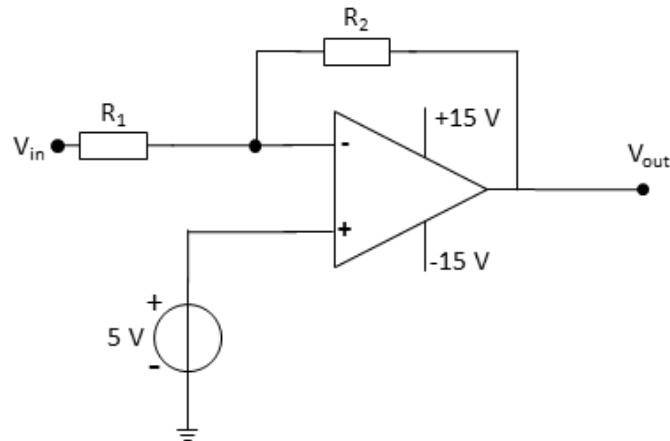
(B) Plot V_{out} versus V_{in} for $-15\text{ V} < V_{in} < +15\text{ V}$ when $\frac{R_2}{R_1} = 2$.



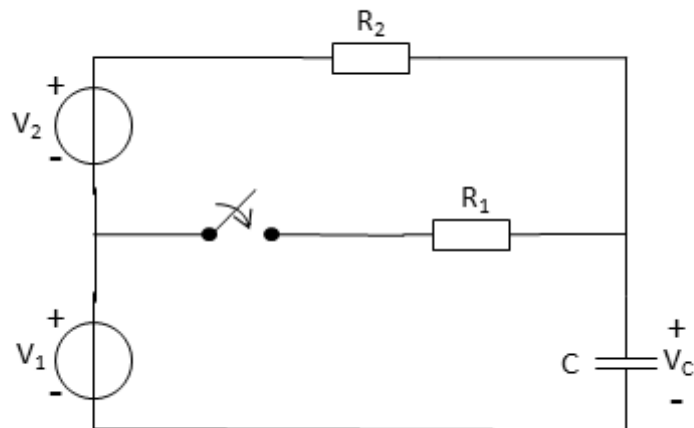
5. The switch has been open for a long time. At $t=0\text{ s}$ the switch closes. Determine the voltage V_c over the capacitor at $t=6\text{ }\mu\text{s}$. $V_1=1\text{ V}$, $V_2=6\text{ V}$, $R_1=10\text{ k}\Omega$, $R_2=15\text{ k}\Omega$ and $C=1\text{ nF}$.



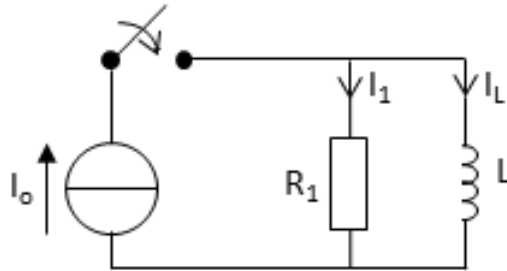6. The switch has been open for a long time. At $t=0$ s the switch closes.
 (A) Derive an expression for the current I_1 as a function I_o , R_1 , L and t .
 (B) Plot $I_1(t)$ for $-3 \mu\text{s} < t < 3 \mu\text{s}$ when $R_1=1 \text{ k}\Omega$, $L=1 \text{ mH}$, $I_o=1 \text{ mA}$.



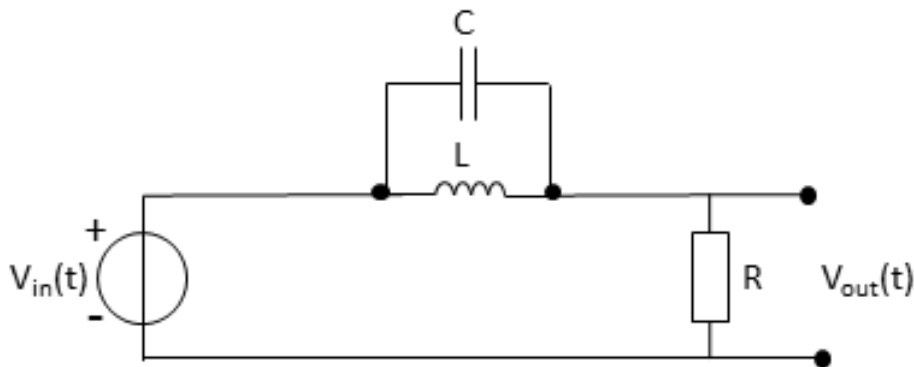7. $v_{in}(t)$ is a steady-state cosine voltage source with amplitude A , angular frequency ω and phase angle ϕ .
 (A) Determine v_{out} when the angular frequency $\omega = \frac{1}{\sqrt{LC}}$.
 (B) What type of filter function does the circuit perform? Motivate your answer.



8. Determine the Thévenin equivalent circuit seen at A-B.
 Draw a schematic of the Thévenin equivalent circuit and express all parameters in the time domain when $\omega=1000 \text{ rad/s}$.

