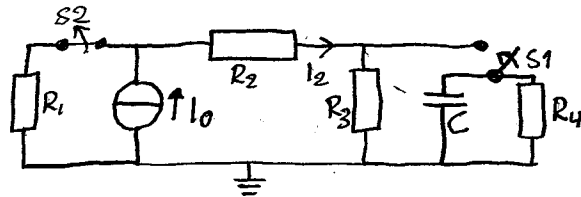


TODAY:



$$\begin{aligned} R_1 &= 1 \text{ k}\Omega \\ R_2 &= 0,5 \text{ k}\Omega \\ R_3 &= 2 \text{ k}\Omega \\ R_4 &= 2 \text{ k}\Omega \\ C &= 3 \mu\text{F} \\ I_0 &= 1 \text{ mA} \end{aligned}$$

S_1 open and S_2 closed for a long time.


At $t_0 = 0 \text{ s}$ S_1 closes

At $t_1 = 2 \text{ ms}$ S_2 opens

Determine the current I_2 in R_2 for all t .

Solution $t < 0 \text{ s}$
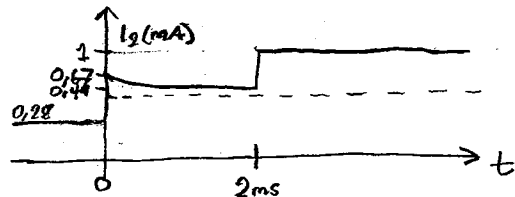
$$I_2 = I_0 \cdot \frac{R_1}{R_1 + R_2 + R_3}$$



$0 < t < 2 \text{ ms}$ Capacitor is now connected $V_C(t)$

What thevenin equivalent does the capacitor see?

$$V_C(t) = V_C(\infty) + (V_C(t_0) - V_C(\infty))e^{-\frac{t-t_0}{\tau}}$$

$$R_{TH} = (R_1 + R_2) // R_3 // R_4 = 0,6 \text{ k}\Omega$$

$$\tau = R_{TH} \cdot C = 1,8 \text{ ms}$$

$$t_0 = 0 \text{ s} \Rightarrow V_C(0) = 0 \text{ V}$$

$$V_C(\infty) = V_{TH} \frac{R_3 // R_4}{(R_1 + R_2) + R_3 // R_4} = I_0 R_1 \frac{R_3 // R_4}{R_1 + R_2 + R_3 // R_4} = 0,4 \text{ V}$$

$$V_C(t) = 0,4 + (0 - 0,4)e^{-t/1,8 \text{ ms}} = 0,4(1 - e^{-t/1,8 \text{ ms}})$$

$$I_2(t) = \frac{I_0 R_1 - V_C(t)}{R_1 + R_2} = \frac{I_0 R_1}{R_1 + R_2} - \frac{I_0 R_1 \cdot R_3 // R_4}{(R_1 + R_2)(R_1 + R_2 + R_3 // R_4)}(1 - e^{-\frac{t}{R_{TH} \cdot C}})$$

$$I_2(t=0) = \frac{I_0 R_1}{R_1 + R_2} = \frac{1}{1,5} = 0,67 \text{ mA}$$

$$I_2(\infty) = \frac{I_0 \cdot R_1}{R_1 + R_2 + R_3 // R_4} = 0,4 \text{ mA}$$

$$I_2(t) = 0,67 - 0,267(1 - e^{-\frac{t}{1,8 \text{ ms}}}) \quad I_2(t=2 \text{ ms}) = 0,67 - 0,267(1 - e^{-\frac{2}{1,8}}) = 0,49 \text{ mA}$$

$t > 2 \text{ ms}$ S_2 Opens

Current in R_2 is determined by current source $I_0 \Rightarrow I_2 = I_0 = 1 \text{ mA}$
(V_C is still continuous and can be calculated for $t > 2 \text{ ms}$.)

P. 7.41 $V_L = L \frac{di_L}{dt} \quad \left[\frac{\text{V}}{\text{A}\cdot\text{s}} \right] = [\Omega \cdot \text{s}] \quad \tau[\text{s}] \quad \tau = \frac{L}{R} = \left[\frac{\Omega \cdot \text{s}}{\Omega} \right] = [\text{s}]$

$$i_L(t) = i_L(\infty) + (i_L(t_0) - i_L(\infty))e^{-\frac{t-t_0}{L/R_{TH}}}$$

Module 4: Sinusoidal R, L, C circuit in steady state

$\sin(t)$ $\cos(t)$

AC sources



$$Z = R + j\omega C$$

$$Z = R + j\omega L$$

Rectangular form $z = a + jb$
Polar form $z = e^{j\theta}$