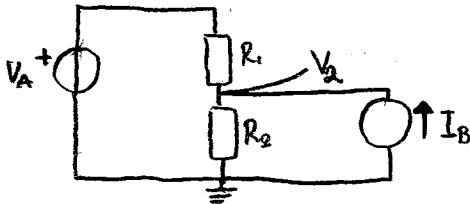


## Superposition


- A linear system obeys the principle of superposition.
- If we have several sources the total response of the circuit is equal to the sum of the responses from each source.

Ex:




Determine  $V_2$

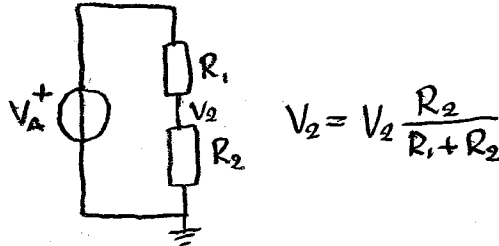- ① Calculate response from  $V_A$  alone. (Turn off  $I_B$ ,  $I_B = 0$  "OPEN")



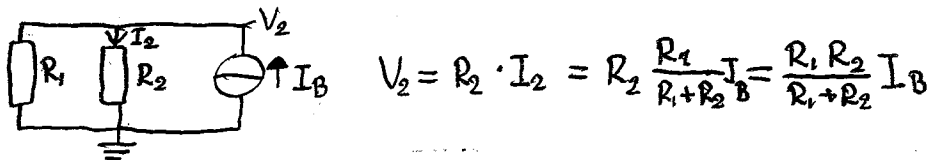- ② Calculate response from  $I_B$  alone (Turn off  $V_A$ ,  $V_A = 0$  "short")



$$\textcircled{1} + \textcircled{2} \quad V_2 = V_A \frac{R_2}{R_1 + R_2} + \frac{R_1 R_2}{R_1 + R_2} I_B$$


Let's do Node-Voltage for comparison

$$\frac{V_A - V_2}{R_1} + \frac{0 - V_2}{R_2} + I_B = 0$$


$$\frac{V_A}{R_1} + I_B = \frac{V_2}{R_1} + \frac{V_2}{R_2} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_2 \Rightarrow V_2 = \frac{1}{R_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} V_A + \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} I_B =$$

$$= \frac{R_1 R_2}{R_1(R_1 + R_2)} V_A + \frac{R_1 R_2}{R_1 + R_2} I_B$$



# Thevenin Equivalents

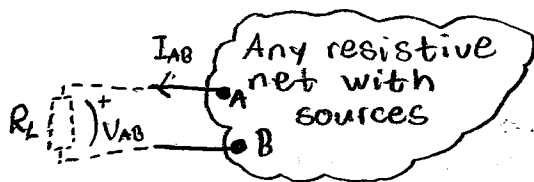

can be described by

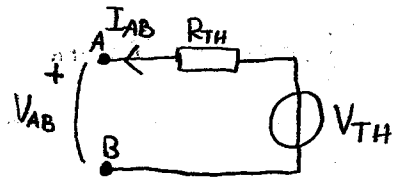

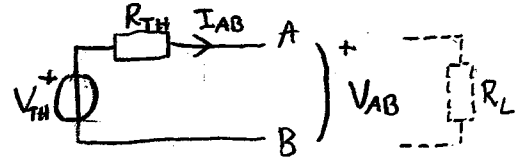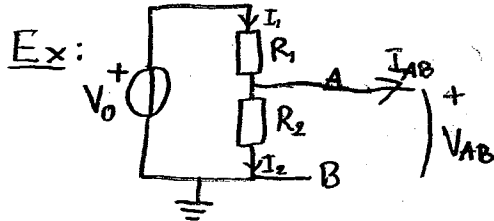if we are only interested in the behavior of the terminals.



$$V_{AB} = V_{TH} - R_{TH} \cdot I_{AB} \quad (1)$$

$$I_{AB} = I_1 - I_2 = \frac{V_0 - V_{AB}}{R_1} - \frac{V_{AB}}{R_2} = \frac{V_0}{R_1} - \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_{AB} = I_{AB} \quad \left( \begin{array}{l} \text{NOTE: if } I_{AB} = I_{SC} \\ \Rightarrow V_{TH} = R_{TH} \cdot I_{SC} \end{array} \right)$$

$$V_{AB} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_0}{R_1} - I_{AB} \Rightarrow V_{AB} = \frac{V_0}{R_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} - \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} I_{AB} = \frac{V_0}{R_1 \left( \frac{R_1 + R_2}{R_1 R_2} \right)} - \frac{1}{\frac{R_1 + R_2}{R_1 R_2}} I_{AB} =$$

$$= \frac{R_2}{R_1 + R_2} V_0 - \frac{R_1 R_2}{R_1 + R_2} I_{AB} \quad (2)$$

Compare (1) and (2)  $\Rightarrow V_{TH} = V_0 \frac{R_2}{R_1 + R_2}$  and  $R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$

This was method ① ALWAYS WORKS!

## Method 2

- We see that if  $I_{AB} = 0$  then  $V_{AB} = V_{TH}$
- We see that if  $I_{AB} = I_{SC}$  (the short circuit current) then  $V_{AB} = 0$  which implies  $R_{TH} = \frac{V_{TH}}{I_{SC}}$

① OPEN  $V_{TH} = V_0 \frac{R_2}{R_1 + R_2}$  ② Short terminals  $I_{SC} = \frac{V_0}{R_1}$

$$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{V_0 \frac{R_2}{R_1 + R_2}}{\frac{V_0}{R_1}} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad R_1 // R_2 \quad \text{ALWAYS WORKS!}$$

## Method 3

- ① OPEN FIND  $V_{TH}$  (Same as in method 2)
- ② Zero all sources (Voltage source is short and current source is open)

Find  $R_{TH}$  looking into the terminals A & B.

$$R_{TH} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$