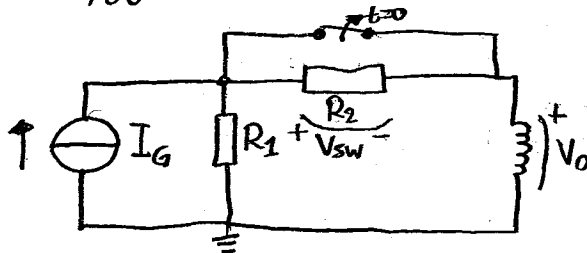


7.41


a) Determine $V_o(t)$

$$V_o = L \frac{di_L}{dt} \quad \text{if I know } i_L \text{ I can calculate } V_o(t)$$

$$t < 0 \quad i_L(t) = I_G \quad i_L \text{ is continuous} \Rightarrow i_L(0) = I_G$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{(t-t_0)}{\tau}}$$

$$i_L(\infty) = I_G \cdot \frac{R_1}{R_1 + R_2}$$


Thevenin resistance seen by L is $R_{TH} = R_1 + R_2 \Rightarrow \tau = \frac{L}{R_{TH}} = \frac{L}{R_1 + R_2}$

$$i_L(t) = I_G \frac{R_1}{R_1 + R_2} + \left(I_G - I_G \frac{R_1}{R_1 + R_2} \right) e^{-\frac{t}{L/(R_1 + R_2)}} = I_G \frac{R_1}{R_1 + R_2} + \left(\frac{I_G R_1 + I_G R_2 - I_G R_1}{R_1 + R_2} \right) e^{-\frac{t}{L/(R_1 + R_2)}} =$$

$$= I_G \frac{R_1}{R_1 + R_2} + I_G \frac{R_2}{R_1 + R_2} e^{-\frac{t}{L/(R_1 + R_2)}}$$

$$V_o(t) = L \frac{di_L}{dt} = L \left(0 + I_G \frac{R_2}{R_1 + R_2} e^{-\frac{t}{L/(R_1 + R_2)}} \cdot \left(-\frac{1}{L/(R_1 + R_2)} \right) \right) = -\frac{I_G R_2}{R_1 + R_2} e^{-\frac{t}{L/(R_1 + R_2)}} =$$

$$= -I_G R_2 e^{-\frac{t}{L/(R_1 + R_2)}}$$

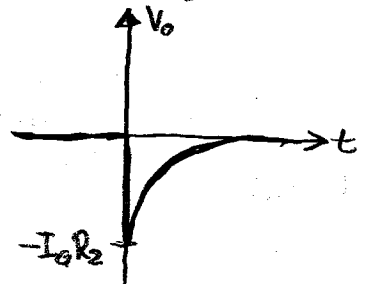 $(i_L(t) > 0, V_o(t) < 0)$ stores energy is delivered to the circuit

b) As R_2 increases the voltage over the inductor increases (as $R_2 \rightarrow \infty \quad V_o \rightarrow -\infty$) in a shorter time $\tau \rightarrow 0 \quad \tau = \frac{L}{R_1 + R_2}$

$$c) \text{ Find } V_{sw}(t) = R_2 \cdot i_L(t) = I_G \frac{R_1}{1 + \frac{R_1}{R_2}} + \frac{I_G R_2}{1 + \frac{R_1}{R_2}} e^{-\frac{t}{L/(R_1 + R_2)}}$$

d) As $R_2 \rightarrow \infty \Rightarrow V_{sw} \rightarrow \infty$ for a short while, A large voltage V_{sw} exist for a time $\tau = \frac{L}{R_1 + R_2}$


Opening an inductive circuit causes a large voltage to be induced over the inductor L . (This large voltage might damage other components)

In the problem 7.41 the large voltage fell over the switch causing it to arc over the switch.

Sinusoidal sources Chapter 9.1-9.3

$$V_s = V_m \cos(\omega t + \phi)$$

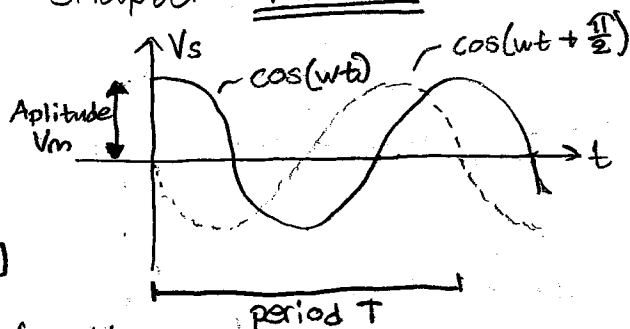Period T , frequency $f = \frac{1}{T} [s^{-1}]$



angular frequency $\omega = 2\pi f [rad/s]$

Amplitude $\pm V_m$ bounds the cos function

ϕ is the phase angle; determines the value at $t=0$

ϕ does not change ω or Amplitude. $\phi > 0$ curve shifts to left
 $\phi < 0$ curve shifts to right

Note ωt and ϕ needs to be the same unit

ω is normally rad

ϕ can be rad but also commonly deg. ($2\pi = 360^\circ$)


• Root Mean Square (RMS) value

$$V_{RMS} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt} = \left\{ \begin{array}{l} \text{for} \\ \text{any} \\ \text{sinusoidal} \end{array} \right\} = \frac{V_m}{\sqrt{2}}$$

also called effective value. The power in a load R having a sinusoidal voltage over it is $P = \frac{V_{RMS}^2}{R}$. ($P = I_{RMS}^2 \cdot R$)

• All waveforms can be built up from summation of sinusoids of different frequency.

Ch. 9.2

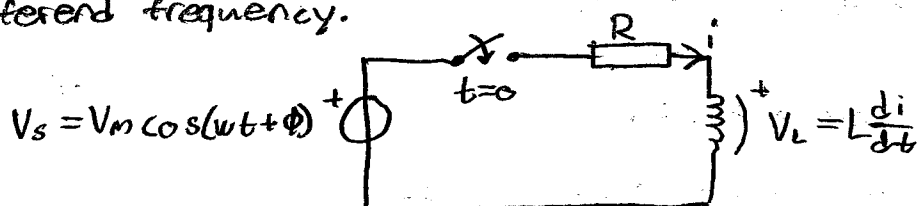

$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$

$$\text{Solving for } i: i(t) = \underbrace{\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-\frac{R}{L}t}}_{\text{Transient}} + \underbrace{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)}_{\text{Steady-state}}$$

$$\theta = \arctan\left(\frac{\omega L}{R}\right)$$

If we are only interested in the steady-state solution we need to determine the amplitude and phase angle in branches/nodes of the circuit. (jw-method).

Note on steady-state solution

- ① A sinusoidal with same frequency as the source (true for linear)
- ② The amplitude generally differs from the source circuits R, L, C
- ③ The phase angle generally differs from the source.