

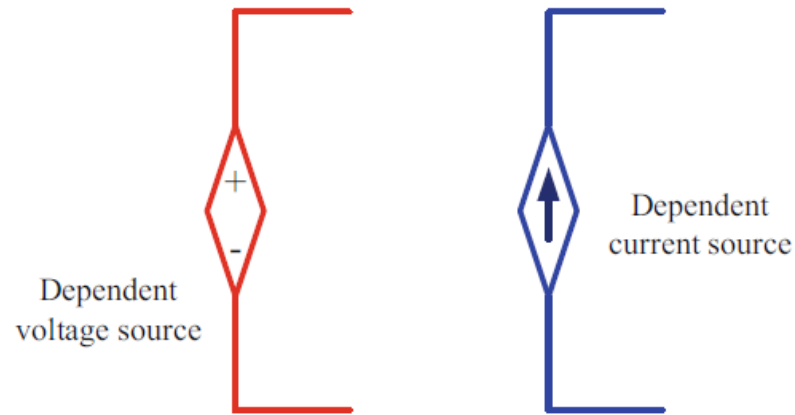



Fig. 1.12 Independent sources

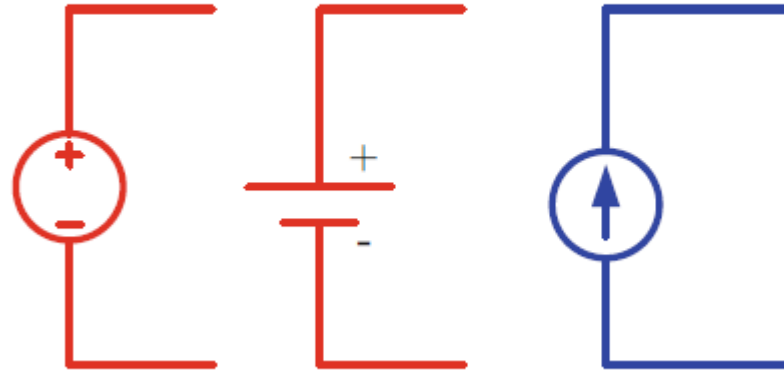

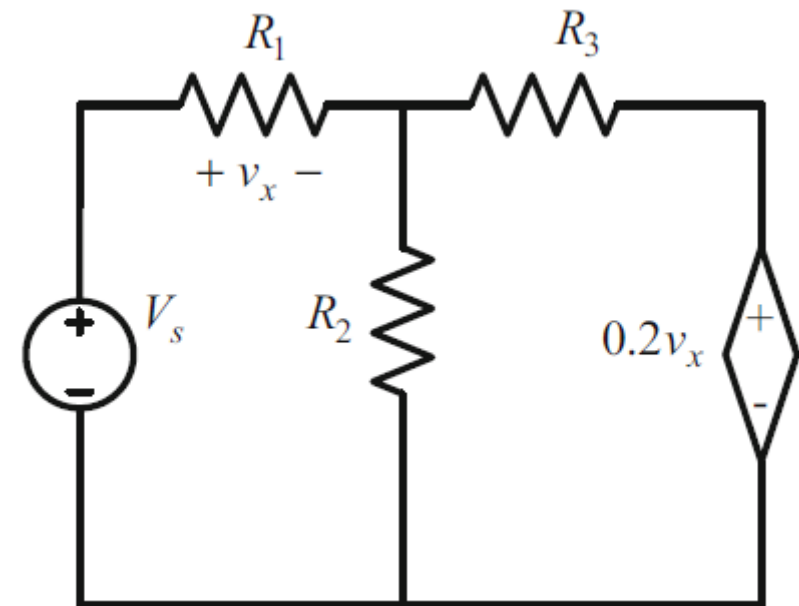- (1) Voltage-controlled voltage source (VCVS)
- (2) Voltage-controlled current source (VCCS)
- (3) Current-controlled voltage source (CCVS)
- (4) Current-controlled current source (CCCS)



Analyze circuits with dependent sources

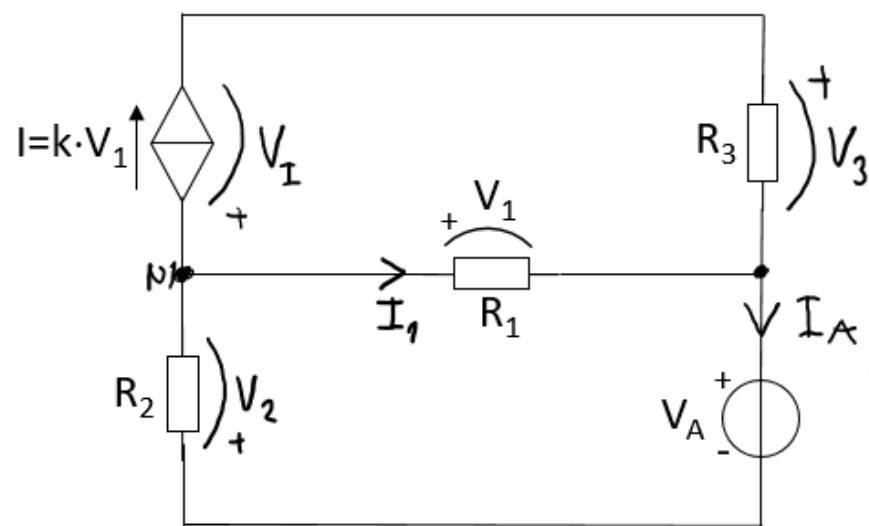

$$R_1 = 2 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega, R_3 = 10 \text{ k}\Omega, V_A = 18 \text{ V}$$

$$k = \frac{1}{3} \text{ mA/V}$$

$$V_I, V_1, V_2, V_3, I_1, I_A, I$$

$$V_3 = R_3 \cdot k \cdot V_1$$

$$\text{KCL in } N_1: \frac{V_1}{R_1} + k V_1 = \frac{V_2}{R_2} \quad (1)$$

$$\text{KVL in lower loop } V_A + V_1 + V_2 = 0 \Rightarrow V_2 = -V_A - V_1 \quad (2)$$

$$(2) \text{ in } (1) \Rightarrow \frac{V_1}{R_1} + k V_1 = \frac{-V_A - V_1}{R_2} \Rightarrow V_1 \left[\frac{1}{R_1} + k + \frac{1}{R_2} \right] = \frac{-V_A}{R_2} \Rightarrow V_1 = \frac{-V_A}{\frac{R_2}{R_1} + k R_2 + 1} = \frac{-18}{\frac{6}{2} + \frac{6}{3} + 1} = -3 \text{ V}$$


$$V_3 = 10 \cdot \frac{1}{3} \cdot (-3) = -10 \text{ V}$$

$$I = k \cdot V_1 = \frac{1}{3} \cdot (-3) = -1 \text{ mA} \quad V_2 = -V_A - V_1 = -18 - (-3) = -15 \text{ V}$$

$$V_1 - V_I - V_3 = 0 \Rightarrow V_I = V_1 - V_3 = -3 - (-10) = 7 \text{ V} \quad I_1 = \frac{V_1}{R_1} = \frac{-3}{2} = -1.5 \text{ mA}$$

$$I_1 + I = I_A \Rightarrow I_A = -1.5 + (-1) = -2.5 \text{ mA}$$

Circuit Element	V [V]	I [mA]	P [mW]
R1	-3	-1.5	4.5
R2	-15	-2.5	37.5
R3	-10	-1	10
I	7	-1	-7
VA	18	-2.5	-45

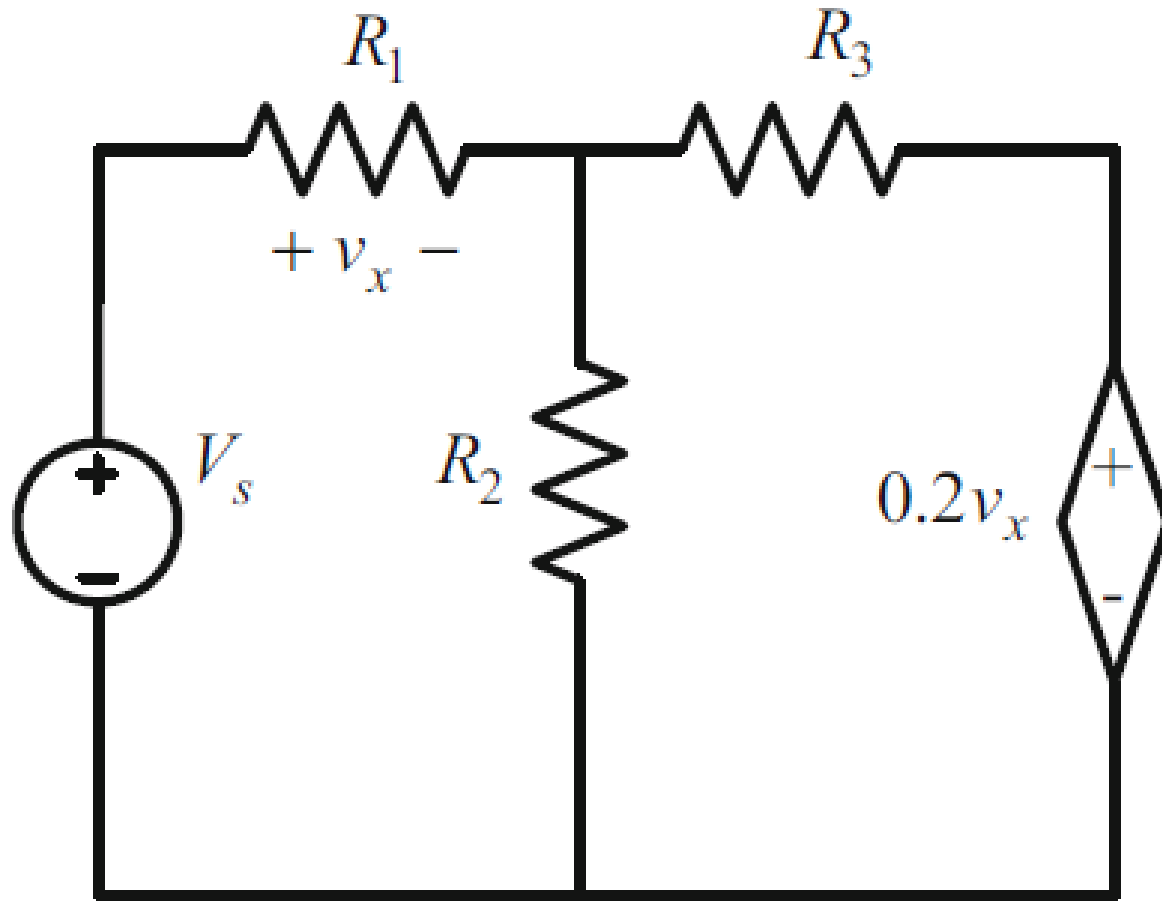

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 2 \text{ k}\Omega$$

$$R_3 = 2 \text{ k}\Omega$$

$$V_s = 10 \text{ V}$$

Determine v_x

Send me an email
(pereh@kth.se) with your
answer and I give you
feedback on your answer.