

$V_s = V_m \cos(\omega t + \phi)$ Phasor representation $\hat{V} = V_m \angle \phi$


$\hat{V} = Z \hat{I}$ Z is impedance $[\Omega]$

Element	$Z[\Omega]$
Resistor	R
Inductor	$j\omega L$
Capacitor	$\frac{1}{j\omega C}$



All linear techniques applies:

- Node-Voltage
- Mesh-Current
- Thevenin-equivalents
- Superposition

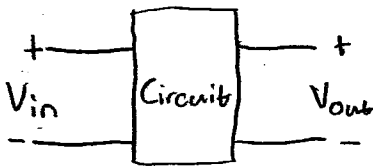Filter circuits (Chapter 14 in book $s = j\omega$)



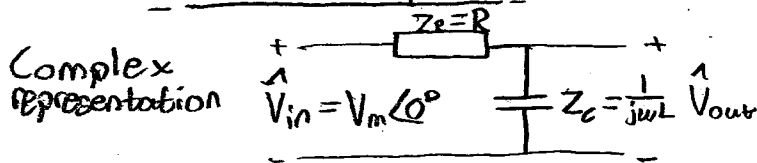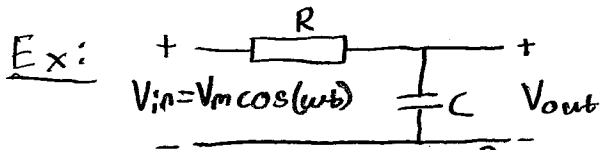- The circuit will change the amplitude and phase angle of V_{out} with respect to V_{in} .
- The amplitude and phase angle of V_{out} will depend on ω of V_{in} .



$$\hat{V}_{out} = \hat{V}_{in} \cdot \frac{Z_C}{Z_R + Z_C} = \hat{V}_{in} \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} =$$


$$= \hat{V}_{in} \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{(1 + j\omega RC)(1 - j\omega RC)} =$$

$$= \hat{V}_{in} \frac{1 - j\omega RC}{1 + (\omega RC)^2}$$

Amplitude ($V_{in} = 1$) $\left| \frac{\hat{V}_{out}}{\hat{V}_{in}} \right| = \left| \frac{1 - j\omega RC}{1 + (\omega RC)^2} \right| = \sqrt{\frac{1}{(1 + (\omega RC)^2)^2 + \frac{(\omega RC)^2}{(1 + (\omega RC)^2)^2}}} = \sqrt{\frac{1 + (\omega RC)^2}{(1 + (\omega RC)^2)^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$

At low frequency $\omega RC \ll 1 \Rightarrow |V_{out}| = |V_{in}|$

At high frequency $\omega RC \gg 1 \Rightarrow |V_{out}| = \frac{|V_{in}|}{\omega RC} \rightarrow 0$ when $\omega \rightarrow \infty$

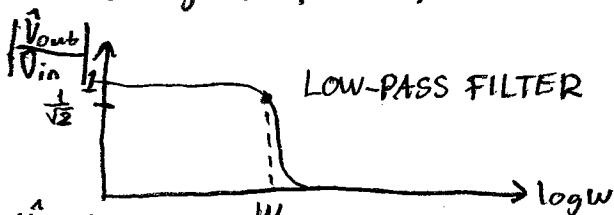

ω_c is the cut-off frequency. $\omega_c = \frac{1}{RC} = \frac{1}{\tau}$

