

Phasor notation (Complex I, V or in Swedish jw-method)

From math Euler's identity $e^{j\theta} = \cos\theta + j\sin\theta$

Thus $V = V_m \cos(\omega t + \phi) = V_m \underbrace{\Re\{e^{j(\omega t + \phi)}\}}_{\text{Real part}} = \Re\{\underbrace{V_m e^{j\phi}}_{\text{This is called the phasor representation of complex } \hat{V}} e^{j\omega t}\}$

$\hat{V} = V_m e^{j\phi}$ contains the amplitude and phase angle information of a given sinusoidal voltage.

The complex number domain is also called the frequency domain since the result depends on frequency ω .

The notation $V_m \angle \phi$ is very common. It is the same as $V_m e^{j\phi}$

Resistor: Assume $i = I_m \cos(\omega t + \phi)$ $\hat{I} = I_m e^{j\phi}$
(R)

$$V = \underbrace{R I_m}_{V_m} \cos(\omega t + \phi) \quad \hat{V} = R \cdot I_m e^{j\phi} = R \hat{I} \text{ Ohm's law.}$$

Inductor L: Assume $i = I_m \cos(\omega t + \phi)$

$$V = L \frac{di}{dt} = L I_m (-\sin(\omega t + \phi)) \cdot \omega = -L I_m \omega \cos(\omega t + \phi - \frac{\pi}{2})$$

$$\Rightarrow \hat{V} = -\omega L I_m e^{j(\phi - \frac{\pi}{2})} = -\omega L I_m e^{j\phi} (\cos \frac{\pi}{2} - j \sin \frac{\pi}{2}) = j\omega L \cdot I_m e^{j\phi} = j\omega L \hat{I} \text{ \{Like Ohm's law, but instead of } R \text{ we have } j\omega L\}}$$

Capacitor:
(C)

$$v = V_m \cos(\omega t + \phi) \quad \hat{V} = V_m e^{j\phi}$$

$$i = C \frac{dv}{dt} = C V_m (-\sin(\omega t + \phi)) \omega = -C \omega V_m \cos(\omega t + \phi - \frac{\pi}{2})$$


$$\Rightarrow \hat{I} = -\omega C V_m e^{j\phi} e^{-j\frac{\pi}{2}} = j\omega C \underbrace{V_m e^{j\phi}}_{\hat{V}} = j\omega C \hat{V}$$

$$\Rightarrow \hat{V} = \frac{1}{j\omega C} \hat{I}$$

Like Ohm's law but instead of R we have $\frac{1}{j\omega C}$

In general we have $\hat{V} = Z \hat{I}$ where Z is called impedance

Element	Z
Resistor	R
Inductor	$j\omega L$
Capacitor	$\frac{1}{j\omega C}$

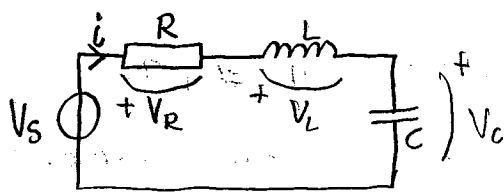


$$V_s = 750 \cos(5000t + 30^\circ)$$

$$R = 90 \Omega \quad L = 32 \text{ mH} \quad C = 5 \mu\text{F}$$

Find i

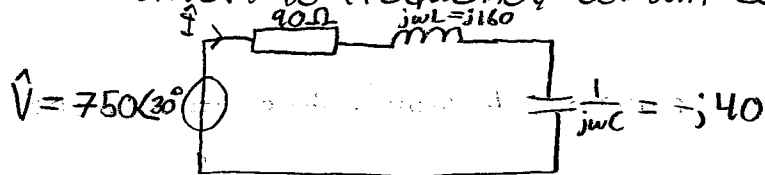Convert to frequency domain equivalent circuit



Impedance seen by the source \hat{V} $Z = R + j\omega L + \frac{1}{j\omega C}$

$$\hat{I} = \frac{\hat{V}}{Z} = \frac{750 \angle 30^\circ}{90 + j160 - j40} = \frac{750 \angle 30^\circ}{90 + j120} = \left\{ \frac{\sqrt{90^2 + 120^2} = 150}{\arctan(\frac{120}{90}) = 53.1^\circ} \right\} = \frac{750 \angle 30^\circ}{150 \angle 53.1^\circ} = 5 \angle -23.1^\circ$$

$$\Rightarrow i(t) = 5 \cos(5000t - 23.1^\circ)$$

Find V_C : $\hat{V}_C = \frac{1}{j\omega C} \hat{I} = -j40 \cdot (5 \angle -23.1^\circ) = 40 \angle -90^\circ \cdot 5 \angle -23.1^\circ = 200 \angle -113.1^\circ$

$$\Rightarrow V_C = 200 \cos(5000t - 113.1^\circ)$$

Find V_L : $\hat{V}_L = j\omega L \cdot \hat{I} = j160 \cdot (5 \angle -23.1^\circ) = 160 \angle 90^\circ \cdot 5 \angle -23.1^\circ = 800 \angle 66.9^\circ$

$$\Rightarrow V_L = 800 \cos(5000t + 66.9^\circ)$$

Find V_R : $\hat{V}_R = R \hat{I} = 90 \angle 0^\circ \cdot 5 \angle -23.1^\circ = 450 \angle -23.1^\circ$

$$\Rightarrow V_R = 450 \cos(5000t - 23.1^\circ)$$