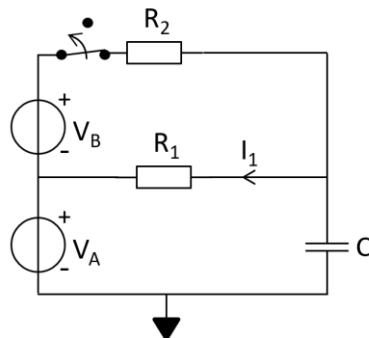



## Home Assignment 5, IE1206 & IF1330, VT2020

### Problem 1



The switch has been closed for a long time. At  $t=0$  s the switch opens. Plot  $I_1(t)$  in the interval  $-1 \mu\text{s} < t < 5 \mu\text{s}$ .  $R_1=1 \text{ k}\Omega$ ,  $R_2=3 \text{ k}\Omega$ ,  $C=0.5 \text{ nF}$ ,  $V_A=1 \text{ V}$  and  $V_B=2 \text{ V}$ .

### Problem 2

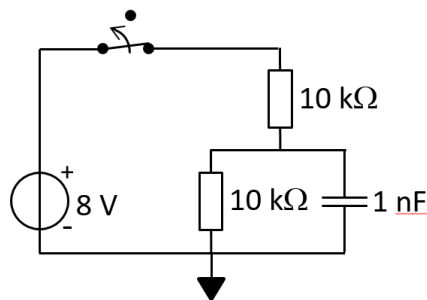


The switch has been closed for a long time and at  $t=0$  s it opens.

(A) What is the energy stored in the capacitor at  $t=0$  s?

(B) At what time is the energy stored in the capacitor 1 nJ?

### Problem 3

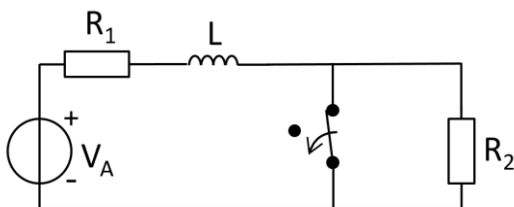


The switch has been closed for a long time. At  $t=0$  s it opens.  $V_A=10 \text{ V}$ ,  $R_1=1 \text{ k}\Omega$ ,  $R_2=100 \text{ k}\Omega$ ,  $L=1 \text{ mH}$ .

(A) What is the voltage over  $R_2$  at  $t=0^+$  s?

(B) What is the time constant  $\tau$  for the inductor to release its stored energy?


#### Problem 4

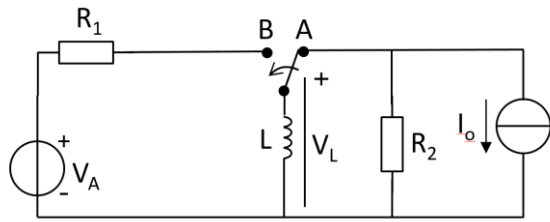

The switch has been in position A for a long time. At  $t=0$  s the switch moves to position B. At what time is the voltage  $V_L$  over the inductor equal to  $V_A$ ?


$R_1=3 \text{ k}\Omega$ ,  $R_2=100 \text{ }\Omega$ ,  $L=10 \text{ mH}$ ,  $I_o=2 \text{ mA}$ ,  $V_A=8 \text{ V}$ .

#### Problem 5

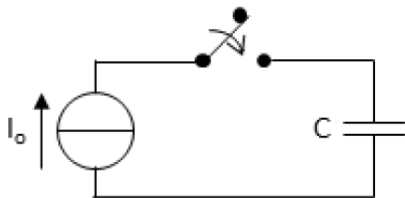

Assume the capacitor is discharged at  $t < 0$  s. At  $t=0$  s the switch closes. Draw a graph showing the voltage over the capacitor,  $V_C(t)$ , in the interval  $-2 \text{ ms} < t < 2 \text{ ms}$ .  $I_o=1 \text{ mA}$  and  $C=1 \text{ }\mu\text{F}$ .

#### Problem 6

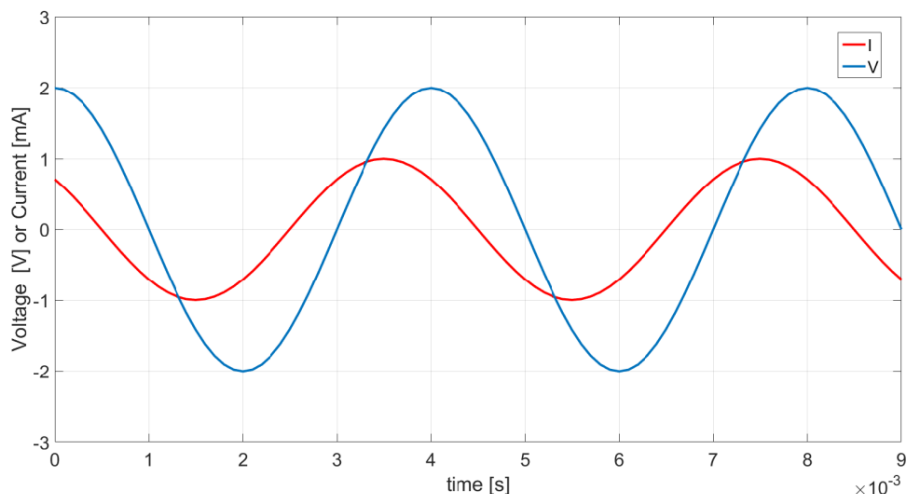

The graph shows an ac voltage (blue) and an ac current (red) as a function of time. Determine the frequency of the voltage and current. Using  $\cos(\omega t)$  as reference determine  $V(t)=V_o\cos(\omega t+\phi_o)$  and  $I(t)=I_o\cos(\omega t+\phi_i)$ . That is determine the amplitude,  $\omega$  and phase angle. Finally write down their representation as complex  $V$  and complex  $I$ .

