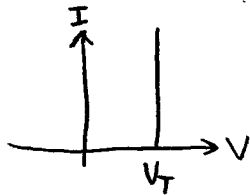


RE Active Components (OP-AMP Diode)


Diode



Ideal voltage source (V_T) in forward direction
 $V_D < V_T$ the diode blocks current ie $I_D = 0A$.

A resistor in series with the diode limits the current!

IDEAL OP-AMP

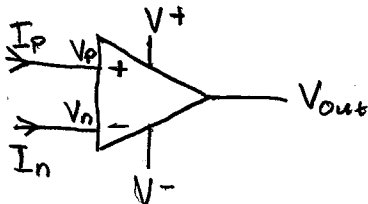

If the op-amp operates in the linear region then $V_n = V_p$ (Ch 5.2 in book)

Using negative feedback we can make the op-amp operate in the linear region.

The input resistance of an ideal op-amp is ∞

$$\Rightarrow I_n = I_p = 0A$$

There is many resistive net configurations to create different circuit functions.


The book describes 4 of them:

- Inverting amplifier
- Summing amplifier
- Non-inverting amplifier
- Difference amplifier

Skills you should aquire

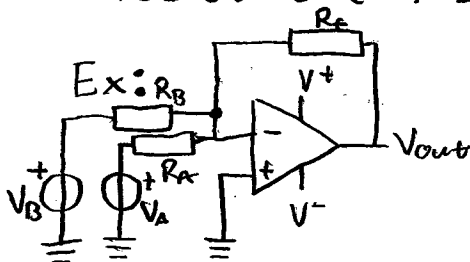Examples 5.1-5.5

- Assuming ideal OP-AMP and assume operation in linear region. derive an expression for V_{out} as a function of all input $V_{in}(V_A, V_B, V_C \dots)$ and all resistors ($R_1, R_2 \dots$).



$$\frac{V_B - 0}{R_B} + \frac{V_A - 0}{R_A} + \frac{V_{out} - 0}{R_F} = 0$$

$$\Rightarrow V_{out} = -\left(\frac{R_F}{R_A} V_A + \frac{R_F}{R_B} V_B\right)$$

The function is to scale and sum V_A and V_B to produce V_{out}

- Evaluate which inputs voltages are allowed to operate in the linear region, i.e. at what input voltages does V_{out} go to saturation V^+ or V^-

Ex again $V^+ = 16V$, $V^- = -16V$, $R_F = 4k\Omega$, $R_A = 2k\Omega$, $R_B = 1k\Omega$, $V_A > 0V$, $V_B > 0V$

$$V_{out} = -(2V_A + 4V_B) \text{ at saturation } V_{out} = -16V \Rightarrow -16 = -2V_A - 4V_B$$

$$\Rightarrow V_B = -\frac{1}{2}V_A + 4$$

