

Course Summary

Embedded Electronics IE1206

Module 1: Resistive Circuits

Ohm's law, KCL and KVL:

Adding two parallel resistors:

$$R_T = \frac{R_1 * R_2}{R_1 + R_2}$$

Voltage division:

V_{R1} = Seeked voltage.

V_S = Voltage source

$$V_{R1} = V_S \left(\frac{R_1}{R_1 + R_2} \right)$$

Current division:

$$I_{R1} = I_T \left(\frac{R_2}{R_1 + R_2} \right)$$

Node Voltage Method

- Assign a potential ($V_1, V_2 \dots V_N$) to all nodes in the circuit
- Assign 0 to one of the nodes (ground)
- Use KCL in ever every node and express the currents in the node potentials
- Solve the equations to find all node potentials ($V_1, V_2 \dots V_N$)
- Determine all voltages and currents from the known potentials ($V_1, V_2 \dots V_N$)

Mesh Current Method

- Assign a mesh current ($I_1, I_2 \dots I_N$) to all loops in the circuit
- Use KVL in the loop and express the voltages in the loop using the defined currents
- Solve the equations to find all the mesh currents
- Determine all voltages and currents from the now known mesh currents

Superposition

- The voltages/currents in the circuit is the sum of the individual contributions from each source in the circuit

Thevenin and Norton Equivalents

1. Open the load resistor.
2. Calculate / measure the open circuit voltage. This is the **Thevenin Voltage (V_{TH})**.
3. Open current sources and short voltage sources.
4. Calculate /measure the Open Circuit Resistance. This is the **Thevenin Resistance (R_{TH})**.

If only independent sources, kill all the sources and find Req by summing all active.

Voltage \rightarrow short

Current \rightarrow open

R_{TH} can always be found by $\frac{V_{TH}}{I_{SC}}$

Operational amplifier:

Currents going in = 0

$$V_{out} = A(V^+ - V^-)$$

$$V_{out} = AV_{in}$$

$$V_{in} = V^+ - V^-$$

When V_{in}^+ increase $\rightarrow V_{out}$ increase

When V_{in}^- increase $\rightarrow V_{out}$ decrease

When V_{in}^+ decrease $\rightarrow V_{out}$ decrease

When V_{in}^- decrease $\rightarrow V_{out}$ increase

Capacitors

$$\text{Energy in capacitor} = \frac{1}{2} CV_c^2$$

Voltage in capacitor is continuous

$$I_c = C \frac{dV_c}{dt}$$

Voltage in capacitor at time t

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty)) e^{-\frac{t}{\tau}}$$

$$\tau = R_{th} * C$$

Passive circuit elements in frequency domain

Phasor transform:

$$Z_R = R \qquad Z_L = j\omega L \qquad Z_C = \frac{1}{j\omega C}$$

$$\hat{V} = Z * \hat{I}$$

$$V_S = V_m \cos(\omega t + \theta)$$

$$\hat{V}_S = V_m \angle \theta$$

Convert from polar to complex

$$V_m(\cos \theta + j \sin \theta)$$

$$e^{jx} = \cos x + j \sin x$$

$$\text{Example: } 56.00 \angle 27.00^\circ = 49.00 + 25.42j$$

$$\text{Example: } 50.00 \angle -90^\circ = 0 - 50j$$

Example:

Frequency for blue curve:

$$f = \frac{1}{T} = \frac{1}{4 * 10^{-3}} = 250 \text{ Hz}$$

Amplitude for blue: 2V

Blue curve peak at $t = 0\text{s}$ so $\theta = 0^\circ$

$$V = 2 \angle 0^\circ = 2$$



