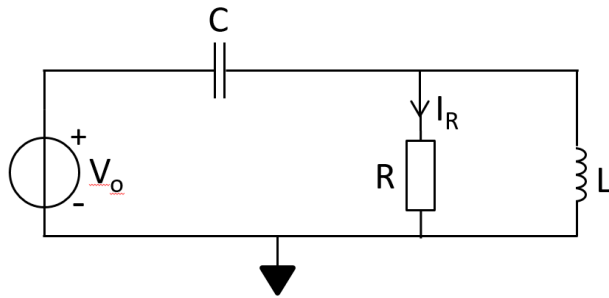



## Home Assignment 6, IE1206 & IF1330, VT2020

### Problem 1




The circuit has a sinusoidal voltage source  $V_o = 5\cos(\omega t)$  V. Determine  $I_R(t)$  when  $\omega = 10^5$  rad/s,  $C = 20$  nF,  $R = 1$  k $\Omega$  and  $L = 10$  mH.

### Problem 2

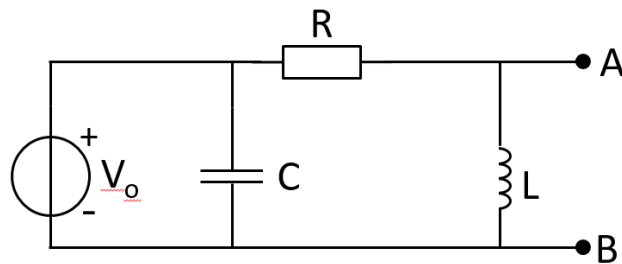


The circuit has a sinusoidal voltage source  $V_o = 5\cos(\omega t + 30^\circ)$  V. Determine the Thévenin equivalent circuit at nodes A-B. The angular frequency  $\omega = 10^6$  rad/s,  $C = 10$  nF,  $R = 100$   $\Omega$  and  $L = 100$   $\mu$ H. Also draw a schematic diagram in time domain with component values of the Thévenin circuit.

### Problem 3

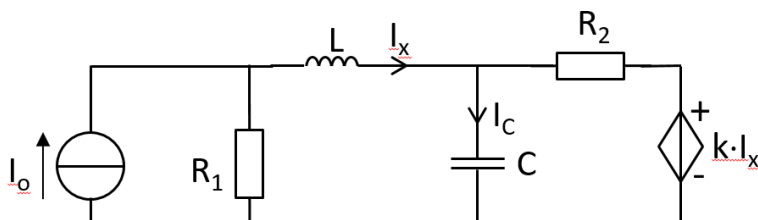


The current source is a sinusoidal source with  $I_o = 3\cos(\omega t)$  mA. Determine the current  $I_C$  when  $R_1 = 2$  k $\Omega$ ,  $R_2 = 6$  k $\Omega$ ,  $C = 25$  nF,  $L = 200$  mH and  $k = 2$  V/mA.

#### Problem 4

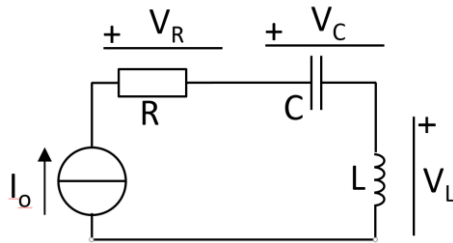

The current source  $I_o = 2\cos(\omega t)$  mA. Determine  $V_R(t)$ ,  $V_C(t)$  and  $V_L(t)$ .  
 $\omega = 10^5$  rad/s,  $R = 1$  k $\Omega$ ,  $L = 20$  mH and  $C = 10$  nF.

#### Problem 5

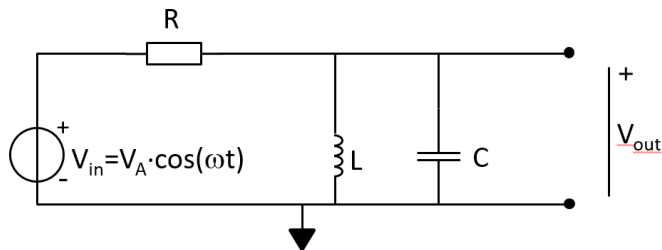


$V_{in}$  is a sinusoidal voltage source. The R,L,C circuit performs a filter function.

(A) Express  $V_{out}$  as a function of  $V_{in}$ ,  $\omega$ ,  $R$ ,  $L$  and  $C$  in the frequency (complex) domain.

(B) Analyse the expression derived in A and motivate what filter function the circuit performs.

(C) At a specific  $\omega$  the output voltage  $V_{out}$  has a maximum amplitude. What is the phase angle of  $V_{out}$  at that frequency?

#### Problem 6

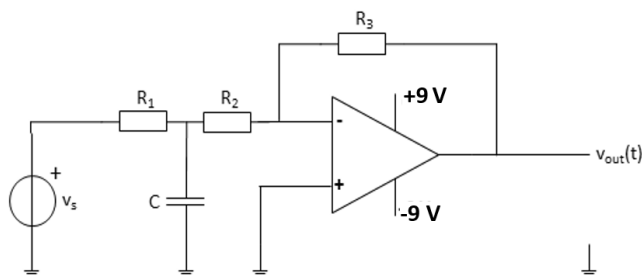

$V_s = 20\cos(5000t)$  [V],  $R_1 = 50$   $\Omega$ ,  $R_2 = 50$   $\Omega$ ,  $R_3 = 65$   $\Omega$ ,  $C = 8$   $\mu$ F. Assume the op-amp is ideal.

(A) Assume that the op-amp operates in the linear region. Determine  $V_{out}(t)$ .

(B) Motivate if the op-amp operates in the linear region or not in (A).

