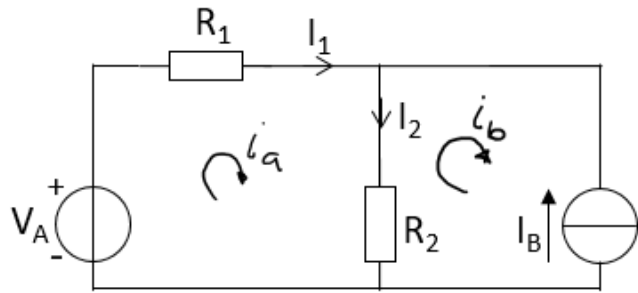


Mesh Current Method

1. Assign a mesh current ($i_1, i_2, i_3, \dots, i_N$) to all loops in the circuit
2. Use KVL in the loop and express the voltages in the loop using the defined mesh currents ($i_1, i_2, i_3, \dots, i_N$)
3. Solve the equations to find all the mesh currents
4. Determine all voltages and currents in the circuit from the now known mesh currents ($i_1, i_2, i_3, \dots, i_N$)



$R_1 = 18 \text{ k}\Omega$, $R_2 = 12 \text{ k}\Omega$
 $V_A = 6 \text{ V}$, $I_B = 3 \text{ mA}$

Determine I_1 and I_2

$$\text{KVL for the left mesh } (i_a): \left. \begin{aligned} V_A - R_1 i_a - R_2 i_a + R_2 i_b &= 0 \\ i_b &= -I_B \end{aligned} \right\} \Rightarrow V_A - (R_1 + R_2) i_a - R_2 I_B = 0$$

$$\Rightarrow i_a = \frac{V_A - R_2 I_B}{R_1 + R_2}$$

$$I_1 = i_a = \frac{V_A}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} I_B = \frac{6}{18+12} - \frac{12}{18+12} 3 = \frac{6-36}{30} = -\frac{30}{30} = -1 \text{ mA}$$

$$I_2 = i_a - i_b = I_1 + I_B = -1 + 3 = 2 \text{ mA}$$

check KVL in left loop: $V_A - R_1 I_1 - R_2 I_2 = 0$
 $6 - 18(-1) - 12 \cdot 2 = 24 - 24 = 0 \quad \checkmark$