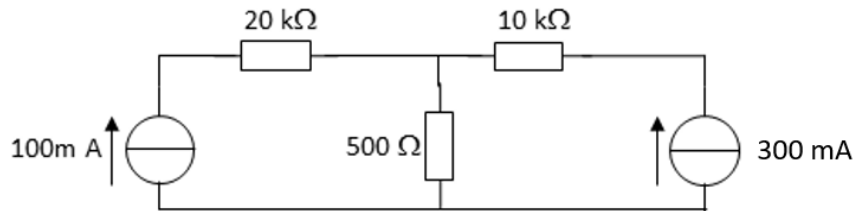



Home Assignment 2, IE1206 & IF1330, VT2020

Problem 1




Determine the total electric energy [J] converted into heat during 1 hour of operation of the circuit.

Problem 2

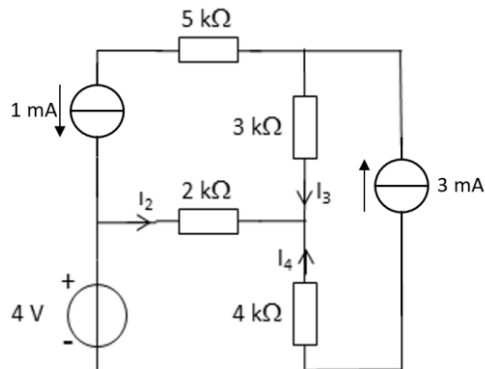


Determine I_2 , I_3 , and I_4 .


Problem 3

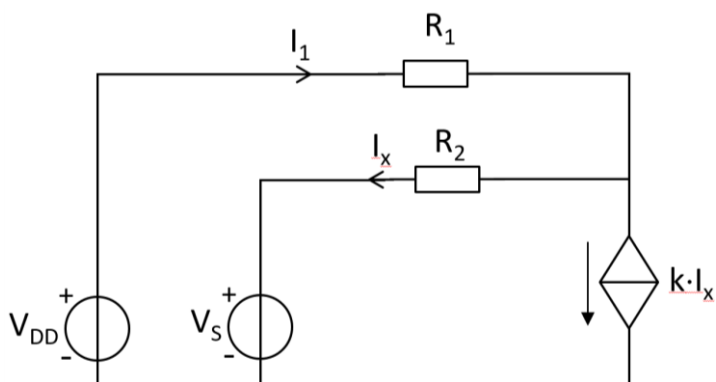


Find an expression for I_1 as a function of V_{DD} , V_S , R_1 , R_2 and k .

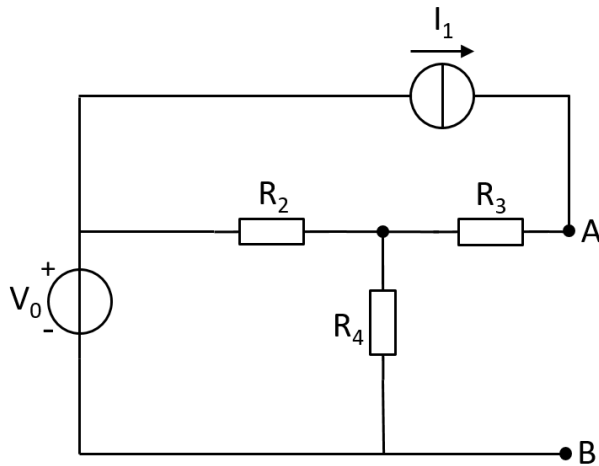Problem 4

Determine the Thévenin equivalent circuit seen at terminals A and B.
 $V_0=22\text{ V}$, $I_1=3\text{ mA}$, $R_2=2\text{ k}\Omega$, $R_3=6\text{ k}\Omega$, $R_4=4\text{ k}\Omega$

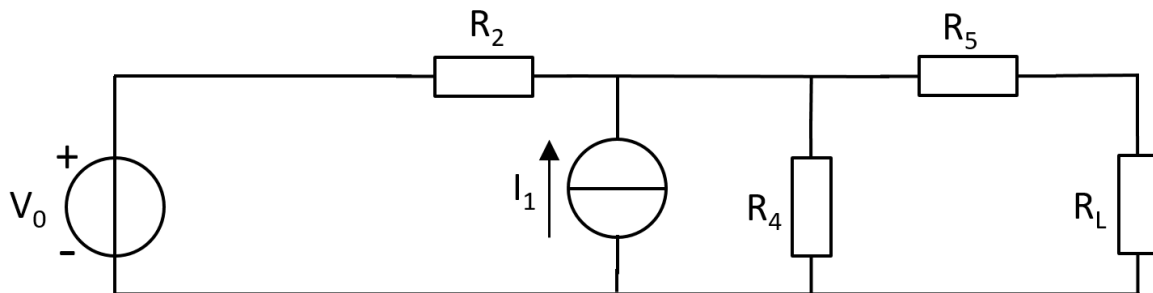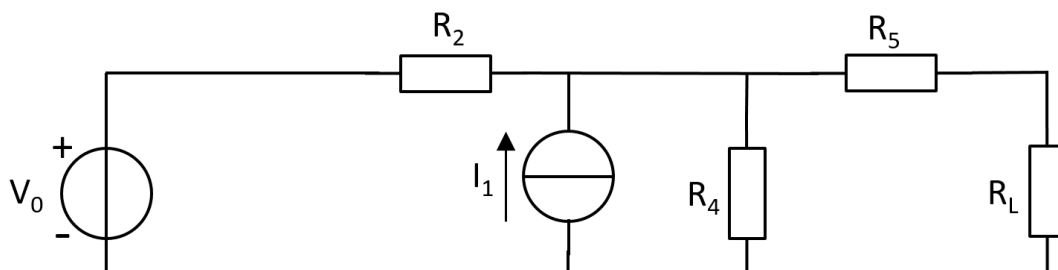Problem 5

What is the Thévenin equivalent circuit seen by the resistor R_L ?
 $V_0=10\text{ V}$, $R_2=5\text{ k}\Omega$, $R_4=5\text{ k}\Omega$, $R_5=7,5\text{ k}\Omega$, $I_1=2\text{ mA}$

Problem 6

$V_0=10\text{ V}$, $R_2=5\text{ k}\Omega$, $R_4=5\text{ k}\Omega$, $R_5=7,5\text{ k}\Omega$, $I_1=2\text{ mA}$
 Determine R_L so that maximum power is consumed in R_L . How much power is consumed in R_L then?

