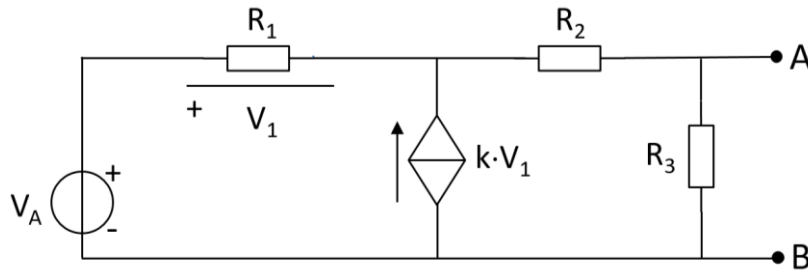



## Home Assignment 3, IE1206 & IF1330, VT2020

### Problem 1



Determine the Thévenin resistance  $R_{TH}$  seen at A-B assuming that  $R_1$ ,  $R_2$ ,  $R_3$ ,  $V_A$  and  $k$  is known.


### Problem 2

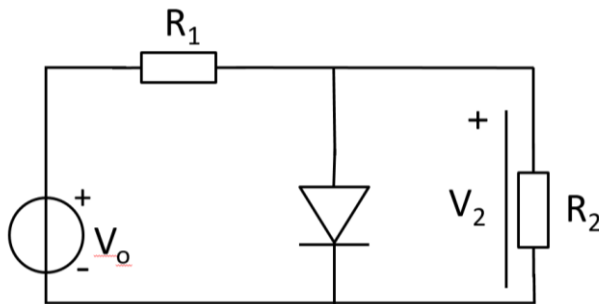


The diode has the forward voltage drop  $V_T$  of 0.7 V and  $R_1 = R_2$ . Determine the voltage  $V_2$  when

- a)  $V_0 = 1$  V      b)  $V_0 = 2$  V      c)  $V_0 = 3$  V.


### Problem 3

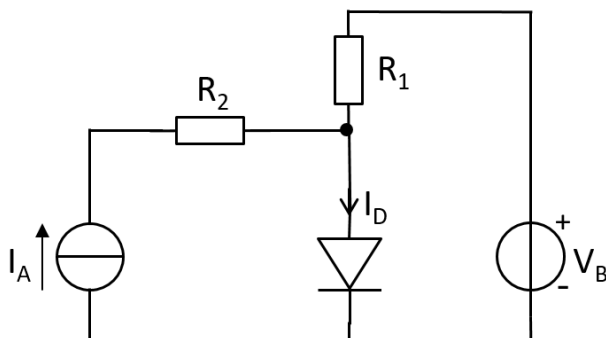

Determine the current  $I_D$  in the silicon diode.  $V_T$  of the diode is 0.7 V.  $V_B = 0.5$  V,  $R_1 = R_2 = 1$  k $\Omega$ .  $I_A = 1$  mA

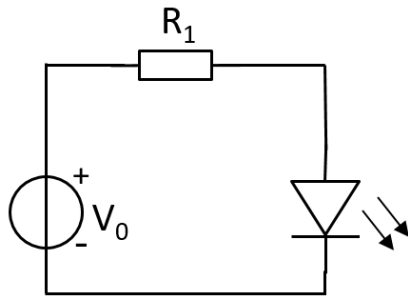**Problem 4**

How much power is consumed in the light emitting diode? The diode emits red color light and has a forward voltage drop of 2 V.  $R_1=1\text{ k}\Omega$  and  $V_0=5\text{ V}$ .

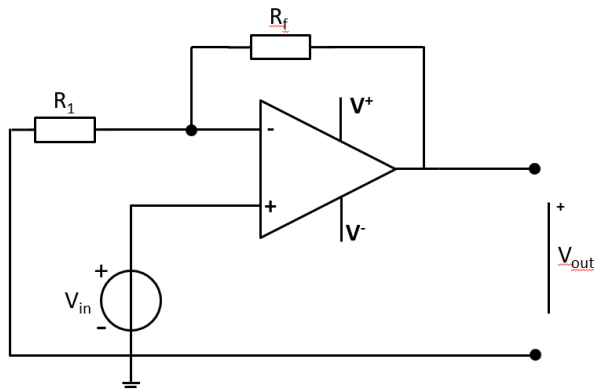**Problem 5**

Assume that the ideal operational amplifier operates in its linear region. With  $R_1$  and  $R_f$  known, derive an expression for  $V_{out}$  as a function of  $V_{in}$

**Problem 6**

$R_1=1\text{ k}\Omega$  and  $R_f=3\text{ k}\Omega$  for the circuit in problem 5.

The supply voltage to the op-amp is  $V^+=12\text{ V}$  och  $V^-=-12\text{ V}$  with respect to ground.

What is  $V_{out}$  if:

a)  $V_{in}=2\text{ V}$

b)  $V_{in}=5\text{ V}$